



University of Engineering & Management, Kolkata

End Semester Examination, November - December, 2022

Programme Name: B.Tech in CSE/CSE(AIML)/CSE(IOT)/CSBS

Semester: 3rd

Course Name: Analog Electronic Circuits

Course Code: ESCE301

Full Marks: 100

Time: 3 Hours

Group - A

Answer 10 questions. Each question carries 2 marks. (2 × 10)

- 1.A. Demonstrate differential amplifier. 2,CO2,Understand
Or
1.B. The slope of DC load line will depend on the value of collector resistor. Explain. 2,CO2,Understand
2.A. Relate the function of regulation in power supply. 2,CO2,Understand
Or
2.B. Explain the parameters cause instability in a Transistor. 2,CO2,Understand
3.A. Explain the names of topologies for negative feedback amplifier. 2,CO2,Understand
Or
3.B. Demonstrate the types of electronic oscillators available. 2,CO2,Understand
4.A. Summarize the application of bias point in brief. 2,CO2,Understand
Or
4.B. Relate the necessity of Transistor Amplifiers in Electronics. 2,CO2,Understand
5.A. Define slew rate of an OPAMP. 2,CO1,Remember
Or
5.B. What are the applications of 555 timer? 2,CO1,Remember
6.A. Define line regulation in brief. 2,CO1,Remember
Or
6.B. List all the basic amplifiers in feedback topologies. 2,CO1,Remember
7.A. Define the Purpose of Filters in a circuit. 2,CO1,Remember
Or

- 7.B. State the Barkhausen criterion for oscillation. 2,CO1,Remember
- 8.A. Explain the full form of Current gain in amplifier. 2,CO1,Remember
- Or
- 8.B. Explain the full form of Voltage gain in amplifier. 2,CO1,Remember
- 9.A. Describe the ripple factor of a Half wave rectifier. 2,CO1,Remember
- Or
- 9.B. State the types of feedback amplifier. 2,CO1,Remember
- 10.A. Sketch the applications of oscillators. 2,CO3,Apply
- Or
- 10.B. Illustrate Multivibrator. 2,CO3,Apply

Group - B

Answer 8 questions. Each question carries 5 marks. (5 × 8)

- 11.A. Reframe the Advantages of RC Coupled Amplifier. 5,CO5,Evaluate
- Or
- 11.B. Evaluate Input Bias Current. 5,CO5,Evaluate
- 12.A. Judge why is 555 timer called so. 5,CO5,Evaluate
- Or
- 12.B. Evaluate the meaning of Feedback fraction. 5,CO5,Evaluate
- 13.A. Discuss where 555 timer is used. 5,CO4,Analyze
- Or
- 13.B. Illustrate the operation of Load Line. 5,CO4,Analyze
- 14.A. Analyze the types of feedbacks present in amplifier. 5,CO4,Analyze
- Or
- 14.B. Categorize positive and negative IC regulators. 5,CO4,Analyze
- 15.A. Show the operation of Series and Shunt feedbacks in amplifier. 5,CO4,Analyze
- Or
- 15.B. Demonstrate a feedback Amplifier. 5,CO4,Analyze
- 16.A. Sketch the frequency response plot of an RC coupled amplifier and explain the same. 5,CO3,Apply
- Or
- 16.B. Show that total gain is equal to the product of gains of individual stages in a multi-stage amplifier. 5,CO3,Apply

17.A. Formulate the key components required in making an oscillator. 5,CO6,Create

Or

17.B. Assesses the Transfer Characteristics curve of Op Amp. 5,CO6,Create

18.A. Classify Time Constant? Define its importance. 5,CO5,Evaluate

Or

18.B. Reframe the disadvantages of RC Coupled Amplifier. 5,CO5,Evaluate

Group - C

Answer 4 questions. Each question carries 10 marks. (10 × 4)

19.A. Design and explain RC coupled amplifier. Sketch a typical frequency response curve. Explain the salient points in it. 10,CO6,Create

Or

19.B. Compile how op-amp can be used as a differentiator. 10,CO6,Create

20.A. Reframe mathematically the ripple factor of a half wave rectifier is 1.21 and full wave rectifier is .48 10,CO5,Evaluate

Or

20.B. Explain the block diagram of op-amp. asses the op amp as an Integrator circuit. 10,CO5,Evaluate

21.A. Classify the reason why voltage divider bias or self bias is better compare to another biasing technique with proper calculation. 10,CO4,Analyze

Or

21.B. Explain the operation of crystal oscillator. 10,CO4,Analyze

22.A. Show, the reason for fixing the operating point in the middle of the load line. also explain how amplification works in Transistor. 10,CO3,Apply

Or

22.B. Sketch and explain full wave center tapped rectifier circuit. show the operation of bridge rectifier. 10,CO3,Apply
