



University of Engineering & Management, Kolkata

Term - II Examination, October - November, 2021

Programme Name: B.Tech in Computer Science

Semester: 3rd

Course Name: Analog Electronic Circuits

Course Code: ESC301

Full Marks: 100

Time: 3 hours

GROUP A (20 Marks)

Answer the following questions. Each question is of 2 marks.

- | | | | |
|----|-------|--|---|
| 1. | i) | Define the Purpose of regulators in a circuits | 2 |
| | ii) | Describe the ripple factor of a full wave rectifier. | 2 |
| | iii) | Relate the necessity of Transistor Amplifiers in Electronics | 2 |
| | iv) | Illustrate the importance of bias stabilization | 2 |
| | v) | Illustrate Why does an op-amp have high CMRR. | 2 |
| | vi) | Demonstrate a voltage follower | 2 |
| | vii) | Examine what is a differential amplifier | 2 |
| | viii) | Define an oscillator . | 2 |
| | ix) | State the Barkhausen criterion for oscillation. | 2 |
| | x) | Classify the meaning of negative feedback? | 2 |

GROUP B (30 Marks)

Answer the following questions. Each question is of 5 marks.

- | | | | |
|-------|-----|---|---|
| 2. | i) | Contrast the differences between filters and regulators. | 3 |
| | ii) | Explain whether a Regulator can convert ac to dc or not. | 2 |
| 3. | i) | Summarize Q point. | 2 |
| | ii) | Classify the factors on which it depends on. | 3 |
| 4. | i) | On the output characteristics of BJT, show the region of operation of (i) an amplifier (ii) a switch. | 5 |
| 5. A. | i) | Judge biasing of BJT and defend need for biasing. | 5 |

OR

- | | | | |
|-------|-----|---|---|
| B. | i) | Explain Load Line. | 3 |
| | ii) | Memorize its Importance | 2 |
| 6. A. | i) | If $ADM = 20000$ and $CMRR = 80$ dB. Then decide the value of ACM | 5 |

OR

- | | | | |
|--------------|-----------|---|----------|
| B. | i) | Explain open loop and close loop configuration of an op amp | 5 |
| 7. A. | i) | Define feedback factor or feedback ratio. | 5 |

OR

- | | | | |
|-----------|-----------|--|----------|
| B. | i) | Discover the advantages of multivibrator | 5 |
|-----------|-----------|--|----------|

GROUP C (50 Marks)

Answer the following questions. Each question is of 10 marks.

- | | | | |
|---------------|------------|--|-----------|
| 8. | i) | Explain the superiority of Voltage divider bias over all other biasing techniques. | 5 |
| | ii) | Solve the purpose of use of Transformers in Power supply circuits with suitable mathematical expression. | 5 |
| 9. | i) | Extract the full working principle of a Half wave rectifier with suitable diagram and explain the ripple factor of it. | 10 |
| 10. A. | i) | Correlate between 7812 , 7912 ic series. | 5 |
| | ii) | Describe the advantages of IC regulators in voltage regulation over series and shunt regulators. | 5 |

OR

- | | | | |
|---------------|------------|--|-----------|
| B. | i) | Show, the reason for fixing the operating point in the middle of the load line | 5 |
| | ii) | Classify the reason why voltage divider bias or self bias is better compare to another biasing technique | 5 |
| 11. A. | i) | Extract the full working principle of a Half wave rectifier with suitable diagram and explain the ripple factor of it. | 10 |

OR

- | | | | |
|---------------|------------|--|-----------|
| B. | i) | Demonstrate biasing of BJT and explain need for biasing. | 10 |
| 12. A. | i) | Explain the block diagram of op-amp. | 5 |
| | ii) | Discover any 5 ideal characteristics of op-amp. | 5 |

OR

- | | | | |
|-----------|------------|---|----------|
| B. | i) | Design a subtractor circuit using OPAMP | 5 |
| | ii) | Draw the equivalent circuit of OPAMP and explain. | 5 |
