



**University of Engineering & Management, Kolkata**

**Term - I Examination, August - September, 2021**

**Programme Name: B.Tech in Computer Science**

**Semester: 3rd**

**Course Name: Analog Electronic Circuits**

**Course Code: ESC301**

**Full Marks: 100**

**Time: 3 hours**

---

**GROUP A (20 Marks)**

**Answer the following questions. Each question is of 2 marks.**

- |    |       |   |   |
|----|-------|---|---|
| 1. | i)    | Define the Purpose of Filters in a circuits                     | 2 |
|    | ii)   | Describe the ripple factor of a Half wave rectifier.            | 2 |
|    | iii)  | Classify the types of rectifiers used for ac to dc conversions. | 2 |
|    | iv)   | Relate the necessity of Transistor Amplifiers in Electronics    | 2 |
|    | v)    | Classify the types of Transistor Biasing.                       | 2 |
|    | vi)   | Summarize the application of Q point in brief                   | 2 |
|    | vii)  | Explain the full form of Voltage gain in amplifier.             | 2 |
|    | viii) | Teach the function of R and C in Amplifiers                     | 2 |
|    | ix)   | Describe the equation for inductive reactance                   | 2 |
|    | x)    | Relate the function of regulation in power supply.              | 2 |

**GROUP B (30 Marks)**

**Answer the following questions. Each question is of 5 marks.**

- |       |     |  |   |
|-------|-----|--|---|
| 2.    | i)  | Describe the working principle of a Step Down Transformer with characteristic equations. | 5 |
| 3.    | i)  | Contrast the differences between filters and regulators.                                 | 3 |
|       | ii) | Explain whether a Regulator can convert ac to dc or not.                                 | 2 |
| 4.    | i)  | Summarize Q point.   | 2 |
|       | ii) | Classify the factors on which it depends on.   | 3 |
| 5. A. | i)  | Sketch the Ripple factor of a Half wave and full wave rectifier.                         | 5 |

**OR**

- |              |            |  |          |
|--------------|------------|--|----------|
| <b>B.</b>    | <b>i)</b>  | Explain Load Line.   | <b>3</b> |
|              | <b>ii)</b> | Memorize its Importance  | <b>2</b> |
| <b>6. A.</b> | <b>i)</b>  | Relate the differences between IC regulators and series and shunt regulators | <b>5</b> |

**OR**

- |              |           |  |          |
|--------------|-----------|--|----------|
| <b>B.</b>    | <b>i)</b> | Contrast the differences between Q point and Operating Point       | <b>5</b> |
| <b>7. A.</b> | <b>i)</b> | Sketch the diagram of a Series regulator and explain its operation | <b>5</b> |

**OR**

- |           |            |  |          |
|-----------|------------|--|----------|
| <b>B.</b> | <b>i)</b>  | categorize IC regulators.                                    | <b>3</b> |
|           | <b>ii)</b> | Contrast the differences between 78XX and 79XX IC regulators | <b>2</b> |

**GROUP C (50 Marks)**

**Answer the following questions. Each question is of 10 marks.**

- |               |            |  |          |
|---------------|------------|--|----------|
| <b>8.</b>     | <b>i)</b>  | Define the importance of Biasing and explain its classifications.                  | <b>5</b> |
|               | <b>ii)</b> | Interpret the circuit diagram of a fixed bias circuit and explain its operation.   | <b>5</b> |
| <b>9.</b>     | <b>i)</b>  | Relate why emitter bias is called a self bias.                                     | <b>5</b> |
|               | <b>ii)</b> | Sketch the details of a emitter biasing circuit and explain its operation.         | <b>5</b> |
| <b>10. A.</b> | <b>i)</b>  | Compare between Self bias and fixed bias.  | <b>5</b> |
|               | <b>ii)</b> | Illustrate the circuit diagram of a voltage divider bias and explain its operation | <b>5</b> |

**OR**

- |               |            |  |           |
|---------------|------------|--|-----------|
| <b>B.</b>     | <b>i)</b>  | Explain the superiority of Voltage divider bias over all other biasing techniques.                                     | <b>5</b>  |
|               | <b>ii)</b> | Solve the purpose of use of Transformers in Power supply circuits with suitable mathematical expression.               | <b>5</b>  |
| <b>11. A.</b> | <b>i)</b>  | Extract the full working principle of a Half wave rectifier with suitable diagram and explain the ripple factor of it. | <b>10</b> |

**OR**

- |           |           |   |           |
|-----------|-----------|---|-----------|
| <b>B.</b> | <b>i)</b> | Illustrate Op amp based series Voltage regulator and explain its operation. | <b>10</b> |
|-----------|-----------|---|-----------|

- |               |            |   |          |
|---------------|------------|---|----------|
| <b>12. A.</b> | <b>i)</b>  | Correlate between 7812 and 7912 ic series.  | <b>5</b> |
|               | <b>ii)</b> | Describes the advantages of IC regulators in voltage regulation over series and shunt regulators. | <b>5</b> |

**OR**

- |           |            |  |          |
|-----------|------------|--|----------|
| <b>B.</b> | <b>i)</b>  | Classify and summerize the working principles of a Pi filter with suitable diagram and mathematical equations. | <b>8</b> |
|           | <b>ii)</b> | Define capacitive reactance.   | <b>2</b> |

\*\*\*\*\*