



Azim

University of Engineering & Management, Kolkata

2<sup>nd</sup> Term Examination, November, 2022

Programme Name: B.Tech ( CSE / CSE (AIML) / CSE (IOT, CYS, BCT) )

Semester: 3rd

Course Name: Analog Electronic Circuits

Course Code: ESC301

Full Marks: 30

Date: 1<sup>st</sup> November, 2022

Time: 11.30 am to 12.30 pm

**GROUP – A (10 marks)**

Answer any five of the following questions. Each question is of 2 marks

5 x 2 = 10

1. i) Explain the full form of Voltage gain in amplifier.
- ii) Teach the functions of L and R in Filters
- iii) Write the Purpose of regulators in a circuits
- iv) Design Open loop Gain of Op Amp
- v) Evaluate feedback fraction in amplifier
- vi) Discover the definition of CMRR.

**GROUP – B (10 marks)**

Answer any two the following questions. Each question is of 5 marks

2 x 5 = 10

2. Show the operation of Series and Shunt feedbacks in amplifier.
3. Design Hartley Oscillator in brief.
4. Explain open loop and close loop configuration of an op amp
5. If  $ADM = 25000$  and  $CMRR = 100 \text{ dB}$ . Then decide the value of  $ACM$

**GROUP - C (10 Marks)**

**Answer any one of the following questions. The question is of 10 marks**

**1 x 10 = 10**

6. Explain the operation of RC phase shift Oscillator. What is a Tank Circuit?
7. Point out the Voltage Series Feedback and voltage shunt feedback circuit and explain its operation
8. Define a method to add voltages together and amplify the same with the help of op-amp
9. The non-inverting amplifier circuit using OPAMP has  $R_1 = 2\text{ K}$  and  $R_f = 5\text{ K}$ . Construct the voltage gain of the circuit if input voltage is 5V? Take Example of a standard Non-Inverting Amplifier as Circuit example.

\*\*\*\*\*