



University of Engineering & Management, Kolkata

1st Term Examination, September, 2022

Programme Name: B.Tech (CSE / CSE (AIML) / CSE (IOT, CYS, BCT))

Semester: 3rd

Course Name: Digital Electronics

Course Code: ESC302

Full Marks: 30

Date: 23rd September, 2022 Time: 9.30 am - 10.30 am

GROUP – A (10 marks)

Answer the following questions. Each question is of 2 marks.

5 x 2 = 10

1. i) Convert binary to gray code: $(111011)_2$.
- ii) Convert decimal $(432)_{10}$ to BCD code.
- iii) Demonstrate the subtraction of 10001002 from 10101002 using 2's complement method.
- iv) Design full adder using suitable decoder.
- v) Design full subtractor using 4:1 MUXes and any other logic gates if required.

GROUP – B (10 marks)

Answer the following questions. Each question is of 5 marks.

2 x 5 = 10

2. a) Using K-map, simplify to obtain minimal expression: $Y = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$.
- b) Convert $(52410)_{10}$ to Excess-3 code.
- c) Why DEMUX is known as data distributor? (3+1+1)
3. Design 4:2 priority encoder with output indicator.

GROUP - C (10 Marks)

Answer the following question. The question is of 10 marks.

1 x 10 = 10

4. Derive the characteristic equation and excitation table of JK flip flop.
Convert JK to T flip flop. (3+3+4)
